

## Verilog Assignment -5 Report

Module subtractor(y0, x0, bin, bout, diff) takes a 8-bit input 'x0' and a 8-bit input 'y0' and calculates the difference, we have to call this twice.

We are given a 32 bit input x and we have to find out the value of x/255 which is a 32 bit output y.

We will use  $y = 256y - x$

We will break this 32 bit input x as four bytes as ,  $x_3 = x[0:7]$ ,  $x_2 = x[8:15]$ ,  $x_1 = x[16:23]$  ,  $x_0 = x[24:31]$

Similarly y as  $y = \{y_3, y_2, y_1, y_0\}$ ;

$256 * y$  can be calculated by shifting y to 8 bits left, i.e,  $256y = y_3 y_2 y_1 y_0 00000000$

$256y - x =$   $y_3 y_2 y_1 y_0 00000000$

(-)  $x_3 x_2 x_1 x_0$

-----  
           $y_3 y_2 y_1 y_0$   
-----

Using this logic , we design a Top\_level module to calculate the value of y which takes input as x and outputs y.

We will instantiate the subtractor module 3 times to calculate  $y_2, y_1, y_0$  each at a time.

To calculate the value of  $y_0$  , we will call :

    subtractor sub1(.y0(8'b00000000), .x0(x1), .bin(1'b0), .bout(b1), .diff(y1));

    subtractor sub2(.y0(y1), .x0(x2), .bin(b1), .bout(b2), .diff(y2));

    subtractor sub3(.y0(y2), .x0(x3), .bin(b2), .bout(b3), .diff(y3));

    subtractor sub4(.y0(y3), .x0(x4), .bin(b3), .bout(b4), .diff(y4));

Finally y is the concatenation of  $y_3 y_2 y_1 y_0$  i.e,  $y = \{y_3, y_2, y_1, y_0\}$ .

TestBench.v

Input 1:  $x=510$   $y=2$

Input2:  $x=2550$   $y=10$

